
Boolean Arithmetic

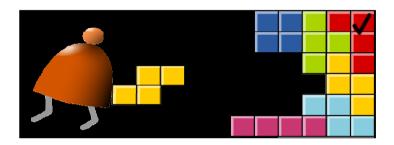

Building a Modern Computer From First Principles
www.nand2tetris.org

Counting systems

quantity	decimal	binary	3-bit register
	0	0	000
*	1	1	001
**	2	10	010
***	3	11	011
***	4	100	100
****	5	101	101
****	6	110	110
*****	7	111	111
*****	8	1000	overflow
******	9	1001	overflow
*****	10	1010	overflow

Rationale


$$(9038)_{ten} = 9 \cdot 10^3 + 0 \cdot 10^2 + 3 \cdot 10^1 + 8 \cdot 10^0 = 9038$$


$$(10011)_{two} = 1 \cdot 2^4 + 0 \cdot 2^3 + 0 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 = 19$$

$$(x_n x_{n-1} ... x_0)_b = \sum_{i=0}^n x_i \cdot b^i$$

Binary addition

Assuming a 4-bit system:

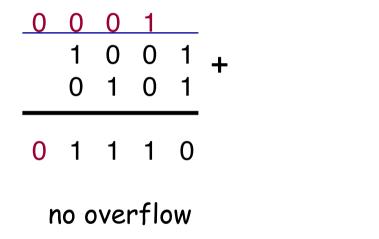

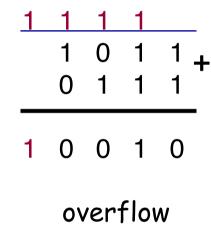

- Algorithm: exactly the same as in decimal addition
- Overflow (MSB carry) has to be dealt with.

Representing negative numbers (4-bit system)

0	0000		
1	0001	1111	-1
2	0010	1110	-2
3	0011	1101	-3
4	0100	1100	-4
5	0101	1011	-5
6	0110	1010	-6
7	0111	1001	-7
		1000	-8


- The codes of all positive numbers begin with a "O"
- The codes of all negative numbers begin with a "1"
- To convert a number: leave all trailing 0's and first 1 intact, and flip all the remaining bits

Example:
$$2-5=2+(-5)=0010$$

$$+1011$$

$$-1101=-3$$

Building an Adder chip

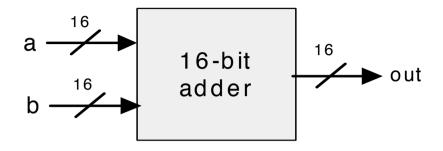

- Adder: a chip designed to add two integers
- Proposed implementation:


Half adder: designed to add 2 bits

• Full adder: designed to add 3 bits

Adder: designed to add two n-bit numbers.

Half adder (designed to add 2 bits)


а	b	sum carry
0	0	0 0
0	1	1 0
1	0	1 0
1	1	0 1

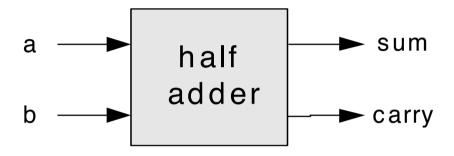

<u>Implementation</u>: based on two gates that you've seen before.


Full adder (designed to add 3 bits)


а	b	С	sum carry	
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

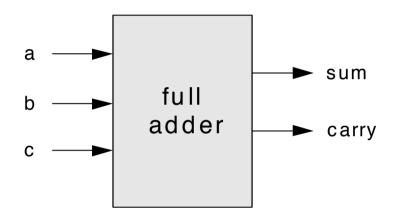

Implementation: can be based on half-adder gates.

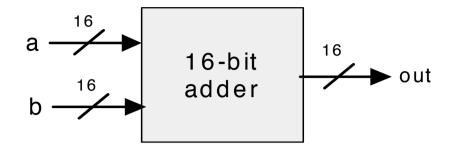
n-bit Adder (designed to add two 16-bit numbers)




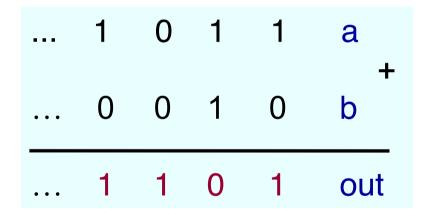

Implementation: array of full-adder gates.

The ALU (of the Hack platform)

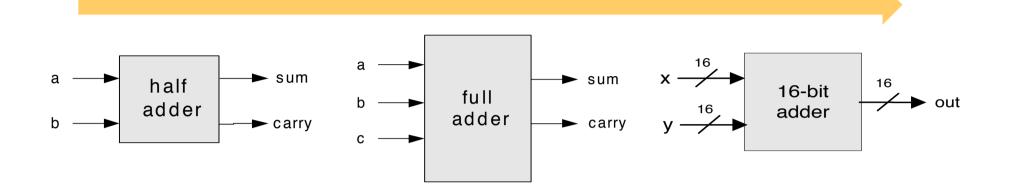


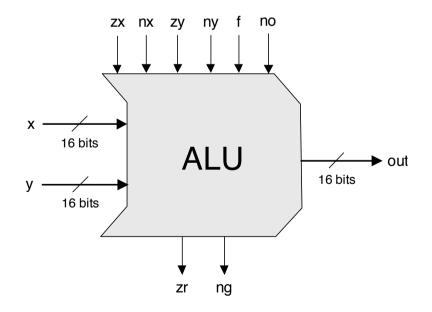

ALU logic (Hack platform)

	These bits instruct how to pre-set the x input		These bits instruct how to The pre-set the y input bet		This bit inst. how to post-set out	Resulting ALU output
zx	nx	zy	ny	f	no	out=
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x And y	if no then out=!out	f(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	٥	1	1	0	Λ	х
1					У	
0	o <u>Implementation</u> : build a logic gate architecture					!x
1	that "executes" the control bit "instructions":					! y
0	o if $zx==1$ then set x to 0 (bit-wise), etc.					-x
1		•				-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	х-у
0	0	0	1	1	1	у-х
0	0	0	0	0	0	х&У
0	1	0	1	0	1	x y

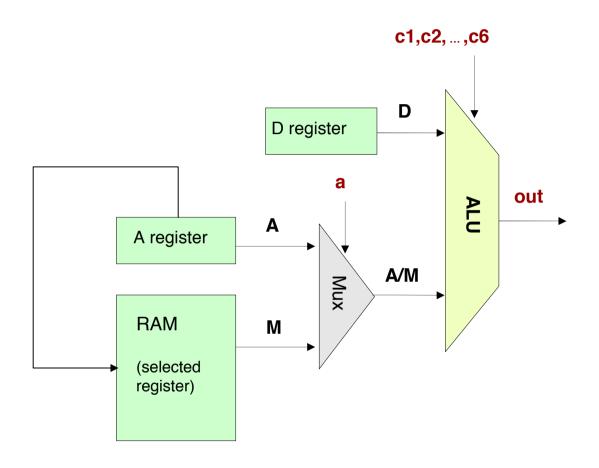The ALU in the CPU context (a sneak preview of the Hack platform)



Perspective

- Combinational logic
- Our adder design is very basic: no parallelism
- It pays to optimize adders
- Our ALU is also very basic: no multiplication, no division
- Where is the seat of more advanced math operations? a typical hardware/software tradeoff.

Historical end-note: Leibnitz (1646-1716)

- "The binary system may be used in place of the decimal system; express all numbers by unity and by nothing"
- 1679: built a mechanical calculator (+, -, *, /)



- CHALLENGE: "All who are occupied with the reading or writing of scientific literature have assuredly very often felt the want of a common scientific language, and regretted the great loss of time and trouble caused by the multiplicity of languages employed in scientific literature:
- SOLUTION: "Characteristica Universalis": a universal, formal, and decidable language of reasoning
- The dream's end: Turing and Gödel in 1930's.





Leibniz's medallion for the Duke of Brunswick